

# Passive Second Order Low Pass Filter

Sam Protsenko

February 9, 2017

## Abstract

Article shows calculating of passive 2nd order LPF (Low Pass Filter) parameters, using Linux software like **Maxima** and **Qucs**.

## 1 Transfer function calculation

### 1.1 Calculating output voltage

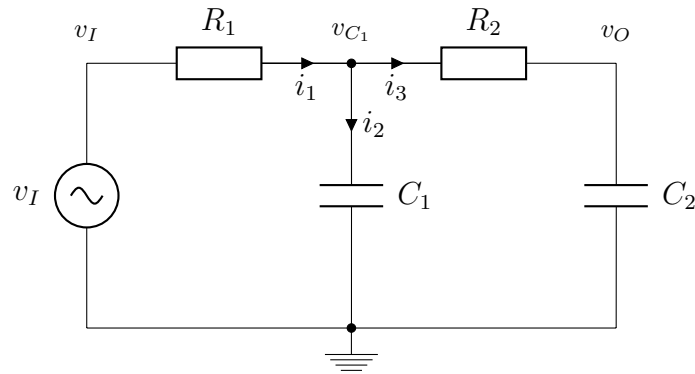


Figure 1: Passive 2nd order LPF

Let's find out  $v_O$  using **node method**. All currents:

$$i_1 = \frac{v_I - v_{C_1}}{R_1}$$

$$i_2 = \frac{v_{C_1}}{X_{C_1}} = \frac{v_{C_1}}{\frac{1}{sC_1}}$$

$$i_3 = \frac{v_{C_1}}{R_2 + X_{C_2}} = \frac{v_{C_1}}{R_2 + \frac{1}{sC_2}}$$

KCL for  $v_{C_1}$  node:

$$i_1 - i_2 - i_3 = 0$$

Substitute currents equations to KCL and solve it for  $v_{C_1}$ :

$$v_{C_1} = v_I \frac{R_2 C_2 s + 1}{(R_1 C_1 s + 1)(R_2 C_2 s + 1) + R_1 C_2 s}$$

Output voltage:

$$v_O = v_{C_1} - i_3 R_2 = v_I \frac{1}{(R_1 C_1 s + 1)(R_2 C_2 s + 1) + R_1 C_2 s}$$

Transfer function:

$$\begin{aligned} H(s) = \frac{v_O}{v_I} &= \frac{1}{(R_1 C_1 s + 1)(R_2 C_2 s + 1) + R_1 C_2 s} \\ &= \frac{1}{R_1 R_2 C_1 C_2 s^2 + (R_1 C_1 + R_1 C_2 + R_2 C_2)s + 1} \\ &= \frac{1}{ms^2 + bs + k} \end{aligned}$$

Where coefficients:

$$\begin{aligned} m &= R_1 R_2 C_1 C_2 \\ b &= R_1 C_1 + R_1 C_2 + R_2 C_2 \\ k &= 1 \end{aligned}$$

Transfer function was calculation in **Maxima**, see listing 1.

#### Listing 1: Transfer function calculation

```
1 i1: (vI - vC1) / R1$
2 i2: vC1 / (1/s/C1)$
3 i3: vC1 / (R2 + 1/s/C2)$
4 eq1: i1 - i2 - i3 = 0$
5 sol: solve(eq1, vC1)$
6 vC1: rhs(sol[1]);
7 i1: ev(i1, sol)$
8 i2: ev(i2, sol)$
9 i3: ev(i3, sol)$
10 vO: ratsimp(vC1 - i3*R2);
11 define(H(s), vO/vI);
```

## 1.2 Standard form of transfer function

Standard form of transfer function for second order LPF:

$$H(s) = \frac{k_{dc}}{\frac{s^2}{\omega_n^2} + 2\frac{\zeta}{\omega_n}s + 1} = \frac{k_{dc}\omega_n^2}{s^2 + 2\zeta\omega_ns + \omega_n^2}$$

Let's calculate coefficients for standard form from our transfer function:

$$\begin{aligned} k_{dc} &= \frac{1}{k} = 1 \\ \omega_n &= \sqrt{\frac{k}{m}} = \frac{1}{\sqrt{R_1R_2C_1C_2}} \\ \zeta &= \frac{b}{2m\sqrt{k/m}} = \frac{R_1C_1 + R_1C_2 + R_2C_2}{2\sqrt{R_1R_2C_1C_2}} \end{aligned}$$

where

- $k_{dc}$  – gain
- $\omega_n$  – natural frequency
- $\zeta$  – damping ratio

Also, quality factor is:

$$Q = \frac{1}{2\zeta} = \frac{m\sqrt{k/m}}{b} = \frac{\sqrt{R_1R_2C_1C_2}}{R_1C_1 + R_1C_2 + R_2C_2}$$

Let's check if calculations are correct so far (see listing 2).

**Listing 2:** Verify if transfer function in standard form is correct

```
1 omega_n: 1 / sqrt(R1*R2*C1*C2)$
2 zeta: (R1*C1+R1*C2+R2*C2) / (2*sqrt(R1*R2*C1*C2))$
3 H(s) := omega_n^2 / (s^2 + 2*zeta*omega_n*s + omega_n^2)$
4 expand(H(s));
```

## 2 Cut-off frequency calculation

From Laplace transform to Fourier transform:

$$H(j\omega) = H(s)|_{s=j\omega} = \frac{\omega_n^2}{-\omega^2 + 2\zeta\omega_nj\omega + \omega_n^2}$$

Real part:

$$\operatorname{Re}(H(j\omega)) = \frac{\omega_n^2(\omega_n^2 - \omega^2)}{(\omega_n^2 - \omega^2)^2 + 4\zeta^2\omega^2\omega_n^2}$$

Imaginary part:

$$\operatorname{Im}(H(j\omega)) = -\frac{2\zeta\omega\omega_n^3}{(\omega_n^2 - \omega^2)^2 + 4\zeta^2\omega^2\omega_n^2}$$

Magnitude:

$$|H(j\omega)| = \sqrt{\operatorname{Re}(H(j\omega))^2 + \operatorname{Im}(H(j\omega))^2} = \frac{\omega_n^2}{\sqrt{(\omega_n^2 - \omega^2)^2 + 4\zeta^2\omega^2\omega_n^2}}$$

Cut-off frequency is where magnitude at *half-power point*, which is  $\frac{1}{\sqrt{2}}$  (approximately at  $-3$  dB):

$$20 \log_{10} K = 20 \log_{10} \frac{1}{\sqrt{2}} \approx -3 \text{ dB}$$

So the equation is:

$$|H(j\omega)| = \frac{1}{\sqrt{2}}$$

$$\frac{\omega_n^2}{\sqrt{(\omega_n^2 - \omega^2)^2 + 4\zeta^2\omega^2\omega_n^2}} = \frac{1}{\sqrt{2}}$$

Solve it for  $\omega = \omega_c$ :

$$\omega_c = \omega_n \sqrt{1 - 2\zeta^2 + \sqrt{4\zeta^4 - 4\zeta^2 + 2}}$$

All calculations were done in Maxima, see listing 3.

#### Listing 3: Calculate cut-off frequency

```

1 _H(s) := omega_n^2 / (s^2 + 2*zeta*omega_n*s + omega_n^2)$
2 H(omega) := subst([s = %i*omega], _H(s))$
3 R(omega) := realpart(H(omega))$
4 X(omega) := imagpart(H(omega))$
5 A(omega) := cabs(H(omega))$
6 /* Print values */
7 H(omega);R(omega);X(omega);A(omega);
8 eq1: A(omega) = 1/sqrt(2)$
9 sol: solve(eq1, omega)$
10 omega_c: rhs(sol[2]);

```

## 3 Simulating the filter

### 3.1 Simplification

To simplify calculations, let's make an assumption:

$$R = R_1 = R_2$$

$$C = C_1 = C_2$$

Then transfer function parameters will be:

$$\omega_n = \frac{1}{RC}$$

$$\zeta = 1.5$$

The quality factor:

$$Q = \frac{1}{3}$$

$Q < \frac{1}{2}$ , so the system is overdamped (doesn't oscillate).

For calculated  $\zeta$  and  $\omega_n$ , we can recalculate out  $\omega_c$ :

$$\omega_c = \frac{\omega_n}{2.672}$$

The cut-off frequency can be calculated:

$$f_c = \frac{\omega_c}{2\pi} = \frac{\omega_n}{16.789} = \frac{1}{16.789RC}$$

### 3.2 RC calculations

Let's calculate  $R$  and  $C$  values for given cut-off frequency:

$$f_c \geq 16 \text{ kHz}$$

Let's choose resistors from E24 series, and capacitors from E6 series, so that  $f_c \geq 16 \text{ kHz}$ :

$$R = 11 \text{ k}\Omega$$

$$C = 330 \text{ pF}$$

Then real cut-off frequency is:

$$f_c = \frac{1}{16.789RC} = 16.408 \text{ kHz}$$

Or in angular form:

$$\omega_c = 2\pi f_c = 103\,094.5 \frac{\text{rad}}{\text{s}}$$

### 3.3 Simulation in Maxima

Listing 4 shows the way to plot bode diagrams in Maxima.

#### Listing 4: Bode plot

```
1 R: 11e3$
2 C: 330e-12$
3 omega_n: 1/R/C$
4 zeta: 1.5$
5 H(s) := omega_n^2 / (s^2 + 2*zeta*omega_n*s + omega_n^2)$
6 load("bode")$
7 omega_from: 2*%pi*100$
8 omega_to: 2*%pi*100000$
9 bode_gain(H(s), [omega, omega_from, omega_to])$
```

The resulting plot is shown on figure 2.

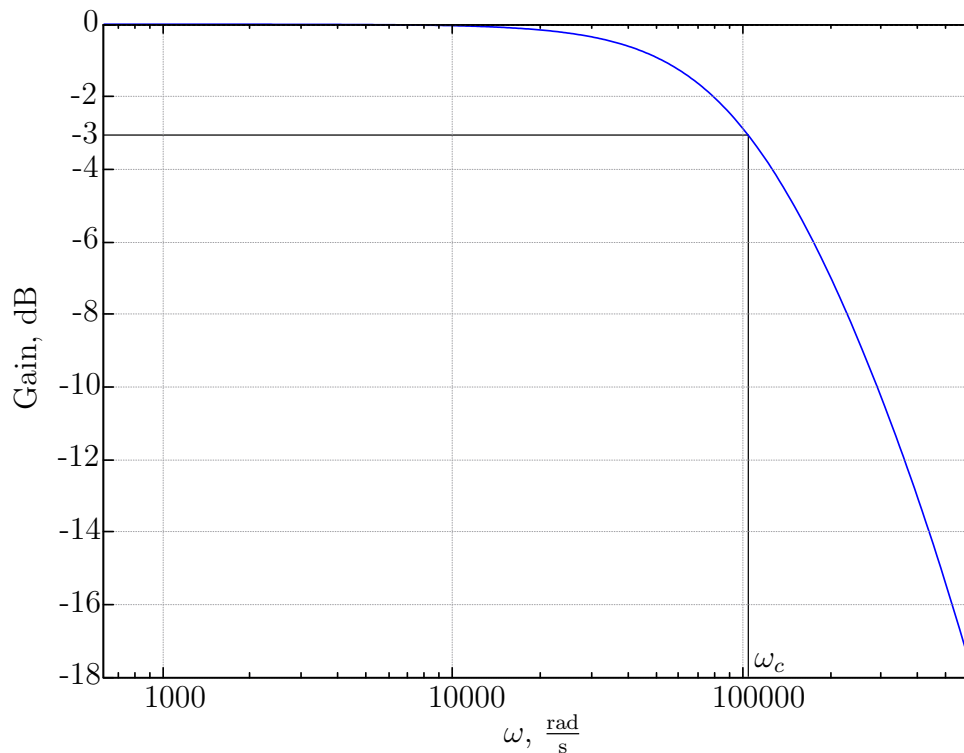


Figure 2: Bode gain plot from Maxima

One can also use COMA package in Maxima for Control Engineering calculations and visualization.

### 3.4 Simulation in Qucs

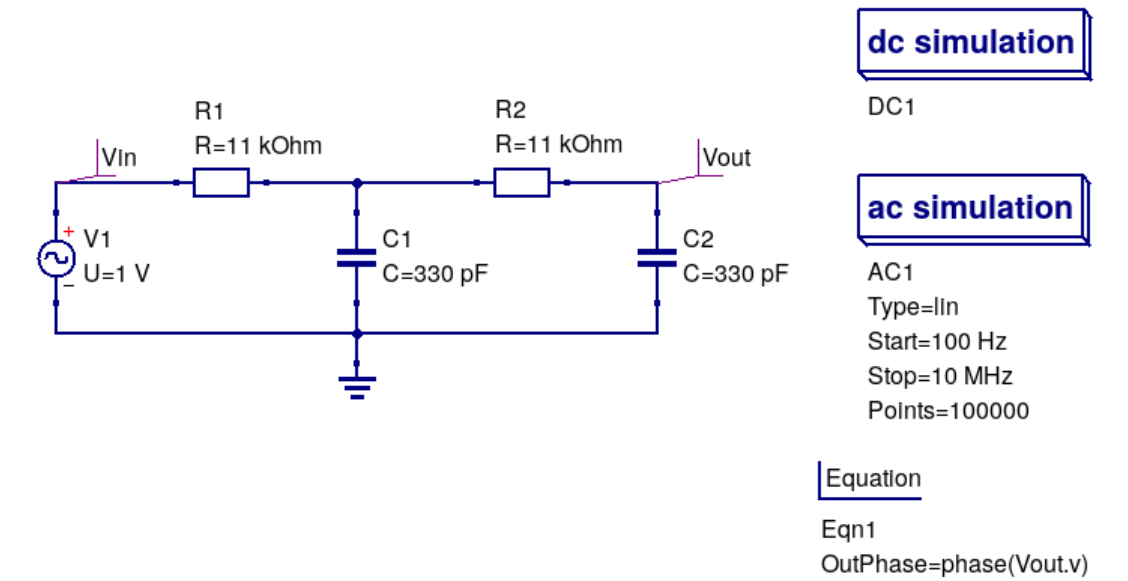


Figure 3: Scheme from Qucs

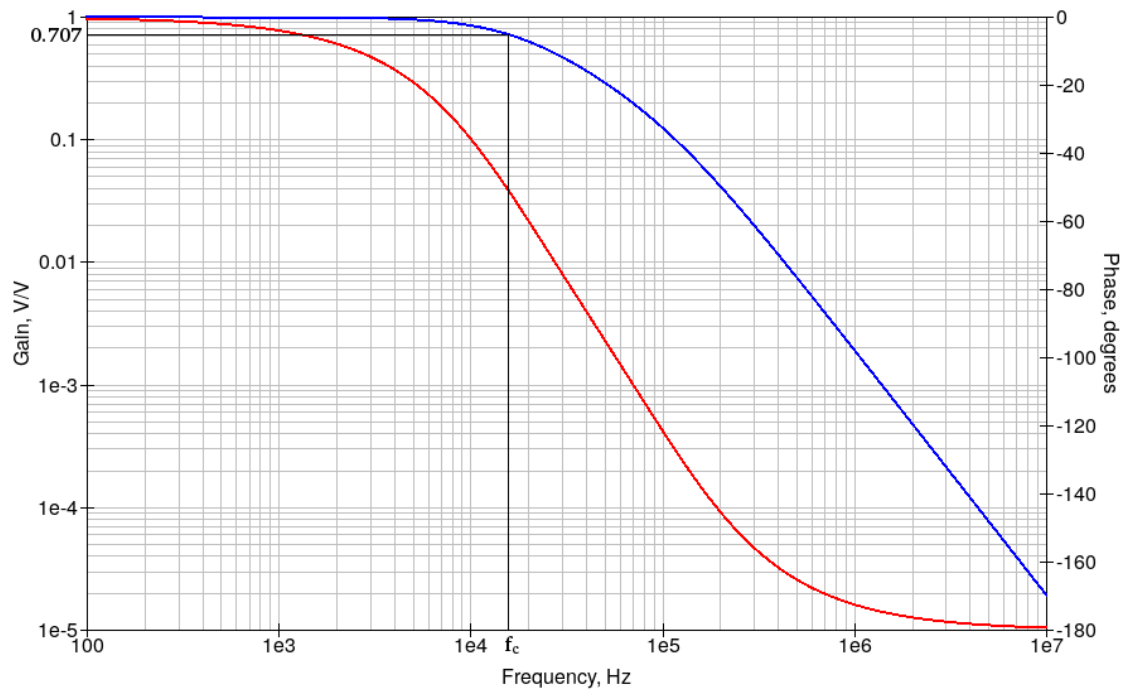


Figure 4: Plot from Qucs